

Designing of Power Management Circuitry for R-PI

e-Yantra Team

July 8, 2015

Contents

1	Objective	3
2	Prerequisites	3
3	Hardware Requirement	3
4	Software Requirement	3
5	Theory and Description	3
5.1	Voltage Supply Unit	3
5.2	uA-7805	4
5.3	LMS-1585a Variable Voltage Regulator	4
5.4	Basic Adjustment for Regulator	5
6	Battery Monitoring	6
6.1	LMS-3914	6
6.2	Use of LM3914 to Monitor 12V	7
7	PCB Designing using OScad	10
7.1	Schematic Design	10
7.2	PCB Layout	10
8	References	11

1 Objective

The objective is to design a Power Management assembly which can perform the following operations:

- Battery voltage monitoring and Smart battery charging
- Regulated supply for on-board payload
- On board Switching from a battery source to an Auxiliary Power Source

2 Prerequisites

One should have:

- Some knowledge about the Current and Voltage Laws governing the design of a circuit.
- Some basic information regarding Power requirements of the system. Like current and Voltage ratings of payload attached to the R-pi.
- the concept of the Regulators should be known.

3 Hardware Requirement

1. NiMH battery and Power adapter as an auxiliary source unit.
2. Voltage Regulator ICs Ua-7805, LMS-1585
3. Dot or Bargraph Display driver IC LMS-3914
4. Resistors, Capacitors and Connecting wires

4 Software Requirement

1. OSCAD.
2. Fritzing.

5 Theory and Description

5.1 Voltage Supply Unit

The battery used in this project is a rechargeable 9.6V, 2.1 Ah Nickel Metal Hydride battery which can power the R-pi assembly for approximately 2 hours. The output of this battery is used to drive R-pi and Payload attached

to it. the payload are Sensors, Motors, port expander IC' s or ADC IC' s and display units like LCD. They generally depend on the type of application. These components use different supplies and hence the output from the battery are dropped and regulated to appropriate level using the regulators to obtain the desired output Voltage Level. In this section regulators used are discussed in brief.

5.2 μ A-7805

This series of fixed-voltage Regulators are designed for a wide range applications. These applications include on-card regulation for elimination of noise and distribution. These regulators can deliver up to 1.5 A of output current.

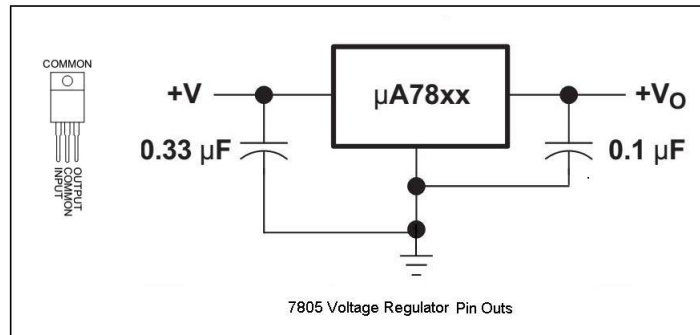


Figure 1: 7805 Voltage Regulator

Some of the features of this regulator are listed as follows

- 3-Terminal Regulators.
- Output Current up to 1.5 A.
- Internal Thermal-Overload Protection.
- High Power-Dissipation Capability.
- Internal Short-Circuit Current Limiting ability.

5.3 LMS-1585a Variable Voltage Regulator

LMS-1585 voltage Regalators are used to provide 3.3V Supply to the R-pi. The low dropout voltage (1.2V) and fast transient response make them an excellent solution for low voltage microprocessor applications.

The LMS1585A/87 series are available in KTT (TO-263) and NDE (TO-220) packages.

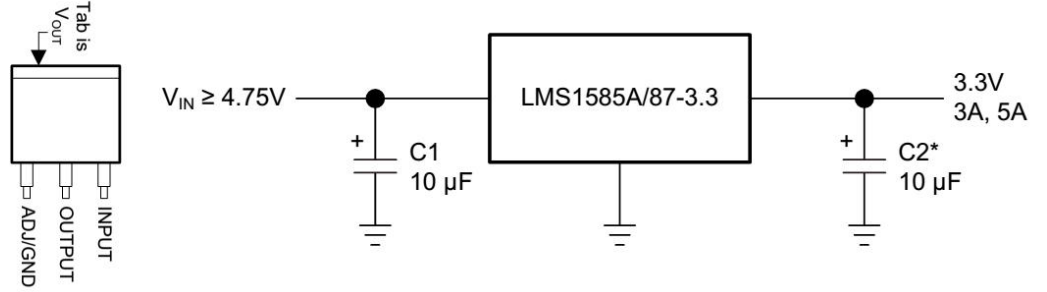


Figure 2: LMS-1585 Voltage Regulator

- The LMS1585A is a low dropout positive regulators with output load current of 3A.
- they offer low dropout voltage (1.2V) and hence fast transient respons
- they are available in adjustable versions, which can set the output voltage with only two external resistors.
- They have built in Current Limiting and Thermal Protection Circuitry.
- Maximum Input to Output Voltage (V_{IN} to GND) 13V and Power Dissipation is Internally Limited

5.4 Basic Adjustment for Regulator

The adjustable version develops at 1.25V reference voltage, (V_{REF}), between the output and the adjust terminal. As shown in Figure 3, this voltage is applied across resistor R_1 to generate a constant current I_1 . This constant current then flows through R_2 . The resulting voltage drop across R_2 adds to the reference voltage to sets the desired output voltage. The current I_{ADJ} from the adjustment terminal introduces an output error. But since it is small (120A max), it becomes negligible when R_1 is in the 100 range. For fixed voltage devices, R_1 and R_2 are integrated inside the devices.

Here we have set the value of resistance $R_1=1.2K \Omega$ and for Output Voltage of 3.3V and We got $R_2=1.96K \Omega$. It is set according to Formula shown in Figure 3.

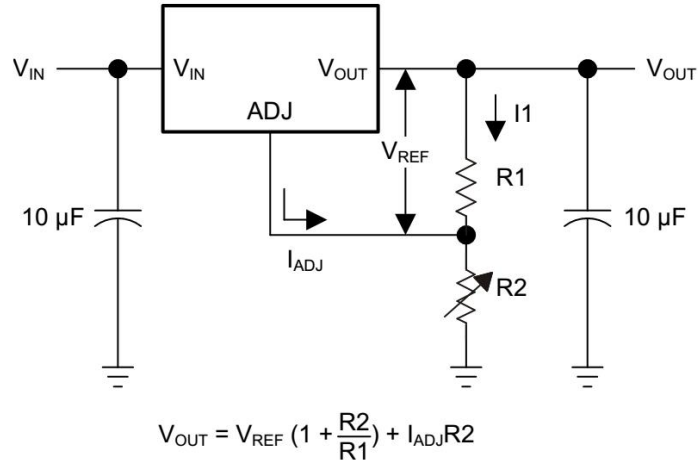


Figure 3: Basic Adjustable Regulator

6 Battery Monitoring

The whole Raspberry-Pi assembly and payload are powered by 9.6V rechargeable Nickel Metal Hydride battery pack. The battery voltage can vary between 12V (fully charged) to 8V (discharged). Battery pack should not be discharged below 8V (1V per cell) for extended battery life.

Note : When the battery reaches full charge, the energy being supplied to the battery is no longer being consumed in the charge reaction, and must be dissipated as heat within the cell. This results in a very sharp increase in both cell temperature and internal pressure. The cell contains a pressure-activated vent which should open if the pressure gets too great, if charging is continued. Further, the Ni-MH cells release hydrogen gas, which will burn violently if ignited.

To prevent Overcharging and fully discharging of the battery a circuitry is required to correctly indicate the user about the voltage levels in the battery for this purpose we have used Texas Instrument manufactured LM3914 dot or bar display driver IC. In this Circuit two LED's are used to indicate full charge indication(12v) and discharge voltage Level(8v).


6.1 LMS-3914

The LM3914 is a monolithic integrated circuit that senses analog voltage levels and drives 10 LEDs, providing a linear analog display. A single pin changes the display from a moving dot to a bargraph. Current drive to the LEDs is regulated and programmable, eliminating the need for resistors. This feature is one that allows operation of the whole system from less than 3V.

Some of the features of this IC are as follows

- Drives LEDs, LCDs or Vacuum Fluorescents.
- this IC can be operated in Bar or Dot Display Mode Externally Selectable by user.
- Internal Voltage Reference from 1.2V to 12V.
- The Internal 10-step Divider is Floating and can be Referenced to a Wide Range of voltages.
- LED Driver Outputs are Current Regulated, open collector ed.

6.2 Use of LM3914 to Monitor 12V

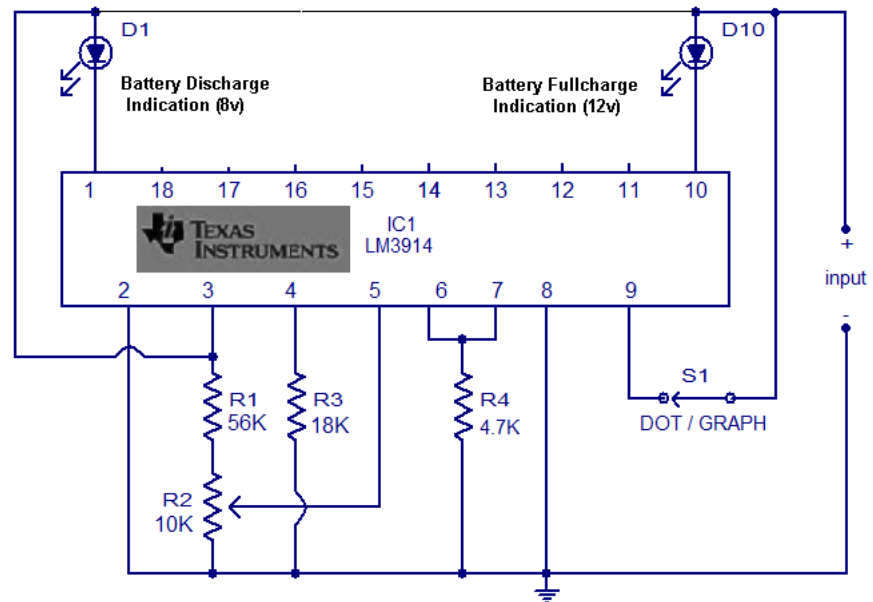

$$\text{Ref Out V} = 1.25 \left(1 + \frac{R2}{R1} \right)$$

$$I_{\text{LED}} \cong \frac{12.5}{R1}$$

Figure 4: LMS-3914 Dot or Bargraph Display Driver

- Switch S1 can be used to select between dot mode and bar graph mode. When S1 is closed, pin9 of the IC gets connected to the positive supply and bar graph mode gets enabled.
- Here the switch is opened to operate the device in dot mode.
- Resistor R4 connected between pins 6,7 and ground controls the brightness of the LEDs. Increasing the value of resistance decreases the brightness of the LED's.
- Resistors R1 and POT R2 forms a voltage divider network and the POT R2 can be used for calibration.
- The upper Limit is calibrated using R2. First the required upper Voltage is set using an Regulated Power Supply unit and by adjusting the pot at R2 the upper Limit is set.
- For adjusting the lower limit, Replace the R1 resistor(s) with a 100K potentiometer (as shown above), connect the desired lower limit voltage to the monitor and adjust the 100K potentiometer until the first red LED just turns on.
- Now replace the Pot by the resistance obtained during calibration.

Note: The circuit Can be powered up by using an auxiliary Source - a 12v adapter . For this change the Position of Switch at Position-2. The Adapter Connected at Auxiliary Power Slot Connects to the Circuit Providing the required supply Voltages. This is indicated in Figure 5 and Figure 6

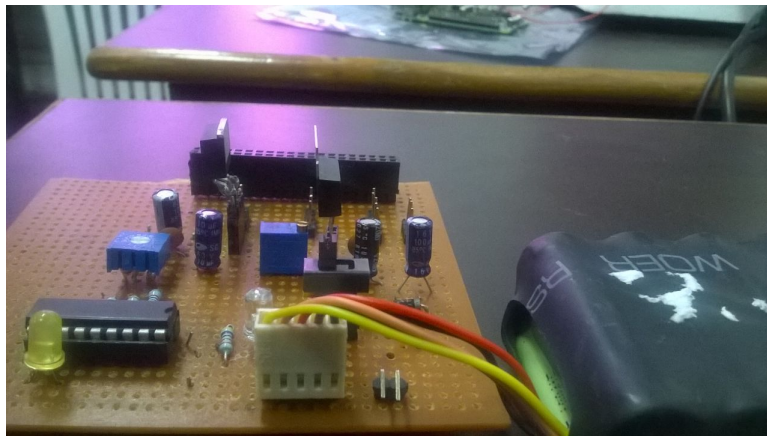


Figure 5: Powering Up of Cicuit Using Battery
Note: Here Switch is at Position-1.



Figure 6: Powering Up of Cicuit Using Adapter
Note: Here Switch is at Position-2.

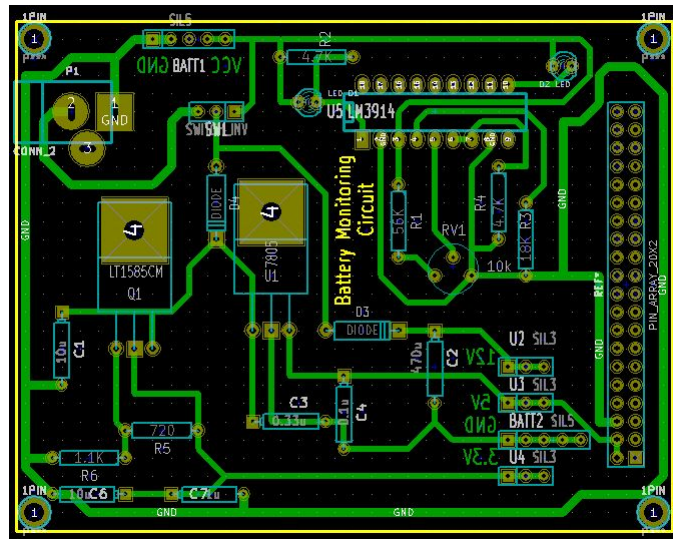


Figure 8: PCB Layout of the Power Management Circuit

8 References

1. Firebird-V Hardware Manual
2. uA7805, LMS1585 and LM3914 Datasheets.
3. http://batteryuniversity.com/learn/article/sharing_battery_knowledge
4. <http://www.ti.com/lit/an/snva557/snva557.pdf>